

EXPERIMENT 5. INTRODUCTION TO VERILOG

I. Introduction

I.I Objectives

In this experiment, you will get familiar with coding with Verilog HDL by designing and implementing basic modules that perform specific set of instructions. Therefore, before coming to lab you should learn and practice about behavioral and structural design with Verilog.

II. Preliminary Work

- 1) Clock enable signals are utilized to enable clocks periodically if the desired hardware operation is slower than the clock signals. Design and implement a clock enabler module similar to the tutorial that enables a given master clock to once in 2, 4 or 8 cycles. The module should have two inputs “clk” and “enabler” and one output “clk_enable”. You should be able to adjust the clock enable factor by changing the value of enabler pin. Block diagram of the module and set of instructions are given below for your convenience.

Value of the division pin	Result
00	No change in the frequency (“dividedclk” should have the same frequency with input “clk”)
01	Input clock should be enabled once in 2 clock signal
10	Input clock should be enabled once in 4 clock signal
11	Input clock should be enabled once in 8 clock signal

 


Fig. 1: Block diagram and instruction sets of the clock divider module.

Include your state diagram, Verilog code, simulation result and RTL schematic of the clock divider module in your preliminary work. You are free to choice input clock frequency in your simulations. Note that you can obtain RTL schematic of a design from **Tools > Netlist Viewers > RTL Viewer**

Note: For both part 2 and part 3 of the preliminary work, you will use hierarchical design. Therefore, if you feel unfamiliar with this topic, please learn about hierarchical design in Verilog before continue on part 2 and 3.

- 2) Design and implement a Verilog module that performs several operations on a given 4 bit data according to instructions taken from a serial port. The top module (consists of three submodules) should have three inputs “clk”, “data” and serial instruction pin “ins” and one serial output pin “serial_out”. The block diagram and instruction set of the top module are given below.


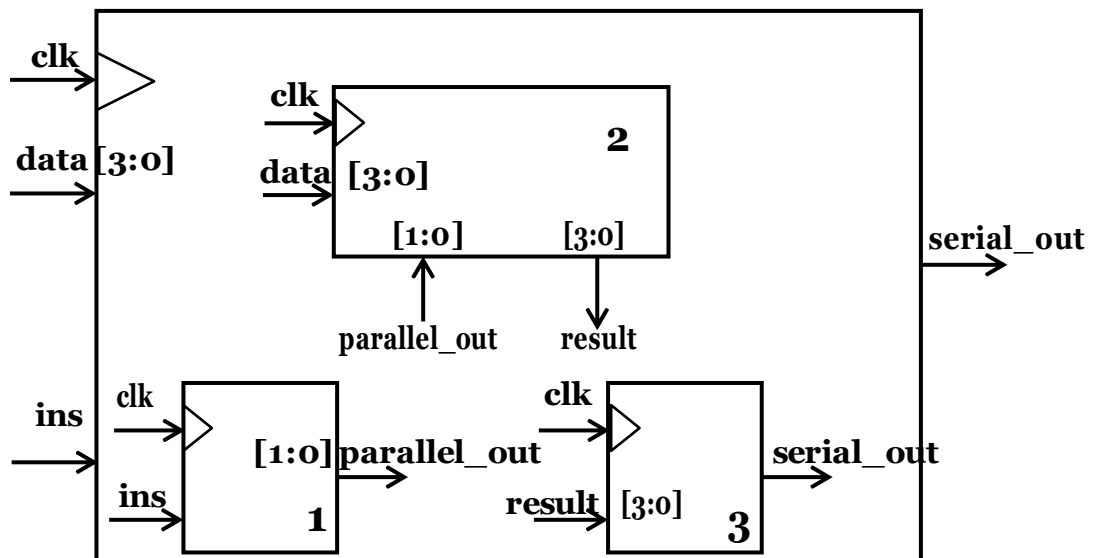


Fig. 2: Block diagram and instruction sets of top module in part 2.

Values read from ins pin	Value of the serial_out pin
00	Number of zeros in the given data (e.g. if data is “0010” the value of serial_out pin should be 0,0,1,1 (represents “3” zeros) respectively.)
01	Right shifted version of the data input by 1 bit
10	1’s complement of the data input
11	Greatest number in a given set of data

 

Signal Name	FPGA Pin No.	Description	I/O Standard
HEX0[0]	PIN_AE26	Seven Segment Digit 0[0]	3.3V
HEX0[1]	PIN_AE27	Seven Segment Digit 0[1]	3.3V
HEX0[2]	PIN_AE28	Seven Segment Digit 0[2]	3.3V
HEX0[3]	PIN_AG27	Seven Segment Digit 0[3]	3.3V
HEX0[4]	PIN_AF28	Seven Segment Digit 0[4]	3.3V
HEX0[5]	PIN_AG28	Seven Segment Digit 0[5]	3.3V
HEX0[6]	PIN_AH28	Seven Segment Digit 0[6]	3.3V

Fig. 4: Connections between seven segment display and pin assignment for the first seven segment digit on FPGA board.

Note that seven segment displays on the FPGA board are active low. Hence, for example; if you want to display the number “1” on the seven segment display, only part 1 and 2 should be ON and therefore only 2nd and 3rd bits of the “display” pin should be LOW (display pin should be equal to “1111001”).

Include state diagrams, Verilog codes, simulation results and RTL schematics of all submodules and the top module you have designed in your preliminary work. You are free to use any clock frequency for the simulation purposes. However, in practice, it will be better to design your module to be worked at a frequency (e.g. 1 Hz) where different random numbers displayed on seven segment display can be recognized with eye. Please note that the clock frequency of the FPGA we use is 50 MHz. Therefore, you may prefer to design a clock enabler that enables the clock once in 1 second.